

113 學年度科技校院四年制與專科學校二年制

統一入學測驗公告答案

考科代碼：4-03-1、4-04-1

類 別：電機與電子群電機類、電機與電子群資電類


考 科：專業科目(一)基本電學、基本電學實習、電子學、電
子學實習

題號	答案	題號	答案	題號	答案	題號	答案	題號	答案	題號	答案
1	B	11	B	21	D	31	D	41	C	51	
2	A	12	A	22	B	32	A	42	B	52	
3	C	13	D	23	A	33	D	43	D	53	
4	C	14	C	24	D	34	A	44	D	54	
5	B	15	B	25	A	35	C	45	D	55	
6	C	16	A	26	A	36	A	46	C	56	
7	B	17	C	27	B	37	A	47	B	57	
8	C	18	B	28	D	38	C	48	C	58	
9	A	19	C	29	A	39	A	49	B	59	
10	D	20	D	30	D	40	C	50	A	60	

$$\begin{aligned}
 1. \quad & V_{c \rightarrow b} = Q(V_b - V_c) \\
 & -20 = Q(10 - 20) \Rightarrow Q = 2C \\
 & V_{a \rightarrow b} = Q(V_b - V_a) \\
 & 64 = 2(10 - V_a) \Rightarrow V_a = -22V \\
 & V_{ca} = V_c - V_a = 20 - (-22) = 42V
 \end{aligned}$$

$$\begin{aligned}
 2. \quad & \begin{array}{l} 20^\circ\text{C} \begin{cases} 20^\circ\text{C} & 10\Omega \\ 40^\circ\text{C} & 11\Omega \\ 80^\circ\text{C} & 13\Omega \end{cases} \end{array} \begin{array}{l} \Delta R \\ 1\Omega \\ 2\Omega \end{array} \\
 & \frac{\Delta R}{\Delta t} = \frac{1}{20} = \frac{2}{40}
 \end{aligned}$$

$$3. \quad V_a = 2 - 2 = 0V$$

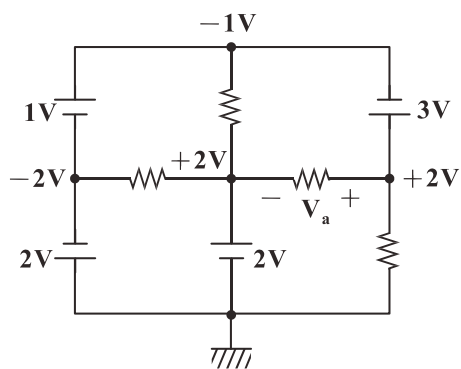

$$4. \quad \text{電橋平衡 } 4 \times 12 = 12 \times 4$$

$$R_T = 1 + 12 // (4 + 4) // (12 + 12) = 1 + \frac{24}{2+3+1} = 1 + 4 = 5\Omega$$


$$I = \frac{10}{5} = 2A$$

$$5. \quad I_1 : I_2 : I_3 = \frac{V_S}{6} : \frac{V_S}{10} : \frac{V_S}{R} = 5 : 3 : 2$$


$$\therefore V_S = 30V$$

$$R = \frac{30}{2} = 15 \Omega$$


$$6. \quad R_{Th} = 4.5 \Omega$$

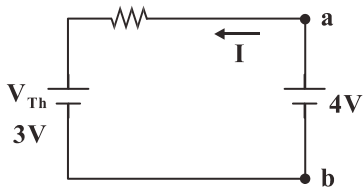
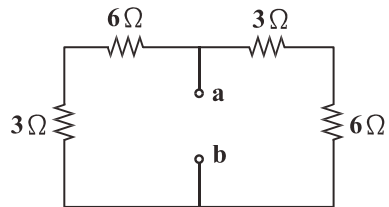
$$R_{Th} = (3 + 6) // (3 + 6) = 4.5 \Omega$$



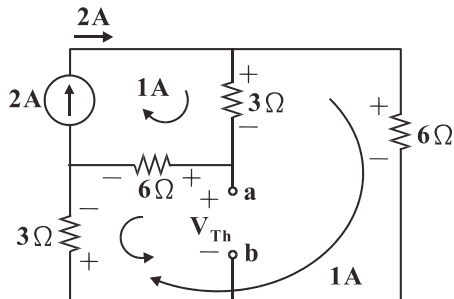
$$V_{Th} = 6 \times 1 - 3 \times 1 = 3V$$




$$I = \frac{4-3}{4.5} = \frac{2}{9} A$$

$$P = 4 \times \frac{2}{9} = \frac{8}{9} W = 0.89W (\text{提供})$$


7.

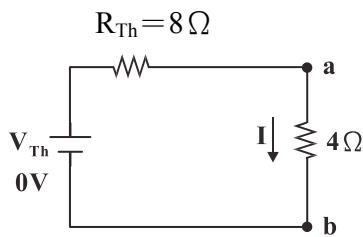

$$R_{Th} = 4 + 2 + 2 = 8\Omega$$

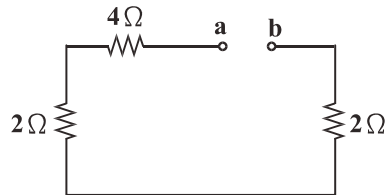

$$V_{Th} = -8 + 4 - 4 + 8 = 0V, I = 0A$$

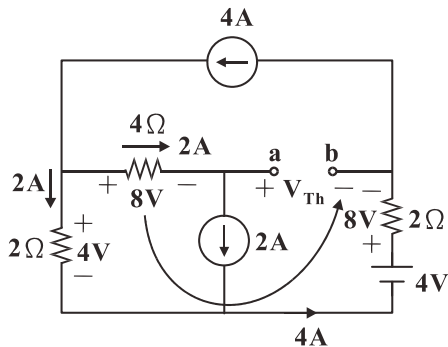


8. $R_{Th} = 3\Omega$

$$V_{Th} = 2 \times 3 + 12 = 18V$$

9. $W_T = \frac{1}{2} L_T I^2 = \frac{1}{2} (4 + 6 + 8 - 2 \times 3 - 2 \times 5 + 2 \times 4) \times 2^2 = 20J$

10. $t = 0^- \quad I(0^-) = \frac{12}{2} = 6A$

$t = 0^+$

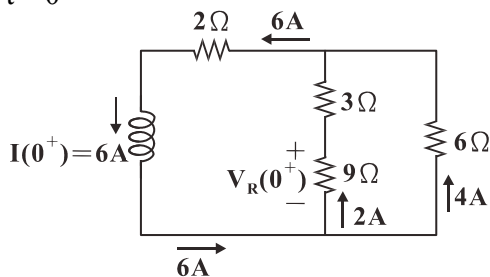

$$V_R(0^+) = -6 \times \frac{6}{12+6} \times 9 = -18V$$

11. $i(t) = -5\cos(100t + 30^\circ)$


$$= 5\sin(100t - 60^\circ)$$

$$-30^\circ - (-60^\circ) = +30^\circ$$

V 超前 I 30°

12. $V_{av} = \frac{15 \times 3}{3+2} = 9V$

13. $j5 + (-j5) = 0\Omega$

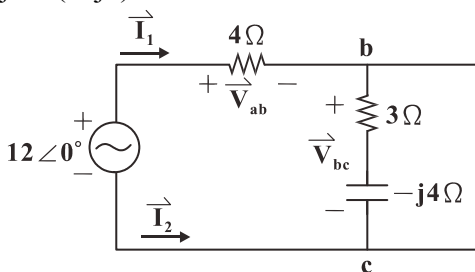

$$\bar{I}_1 = \frac{12\angle 0^\circ}{4} = 3\angle 0^\circ \text{ A}$$

$$\bar{I}_2 = -\bar{I}_1 = 3\angle 180^\circ \text{ A}$$

$$\bar{V}_{ab} = 12\angle 0^\circ \text{ V}$$

14. 串 I 最大 $\Rightarrow$ 諧振時

$$f = 240 \text{ Hz} \quad \begin{cases} X_L = 160\Omega \times \frac{1}{2} \downarrow \\ X_C = 40\Omega \times 2 \uparrow \end{cases}$$

$$f_0 = 120 \text{ Hz} \quad X_{L0} = X_{C0} = 80\Omega$$

$$= 240 \times \frac{1}{2}$$

$$15. \quad BW = \frac{f_0}{Q} = \frac{\frac{1}{2\pi\sqrt{LC}}}{R\sqrt{\frac{C}{L}}} = \frac{1}{2\pi RC}$$

$$\frac{250}{\pi} = \frac{1}{2\pi \times 200 \times C} \Rightarrow C = 10\mu\text{F}$$

$$Q = 200 \sqrt{\frac{10 \times 10^{-6}}{1 \times 10^{-3}}} = 20$$

$$BW = \frac{f_0}{Q} = \frac{f_0}{20} = \frac{250}{\pi}$$

$$f_0 = \frac{5000}{\pi} \text{ Hz} = 1592 \text{ Hz}$$

$$f_1 = 1592 - \frac{250}{2} = 1552 \text{ Hz}$$

$$f_2 = 1592 + \frac{250}{2} = 1632 \text{ Hz}$$

$$16. \quad \triangle \begin{cases} V_\ell = V_P = 25V \\ I_\ell = \sqrt{3} I_P = 8.66 = 5\sqrt{3} \text{ A} \end{cases}$$

$$I_P = 5A$$

$$V_P = 5(3 + j4) = 25V$$

$$P = 3V_P I_P \cos \theta = 3I_P^2 R_P = 3 \times 5^2 \times 3 = 225W$$


$$Q = 3I_P^2 X_P = 3 \times 5^2 \times 4 = 300VAR$$

$$S = 3 \times 5^2 \times 5 = 375VA$$

$$\textcircled{V} = 5(3 + j4) = 25V$$

$$17. \quad \vec{Z} = 3 + (-j4)/(j8) + j10 = 3 + \frac{(-j4)(j8)}{-j4 + j8} + j10 = 3 - j8 + j10 = 3 + j2 \Omega$$

18.

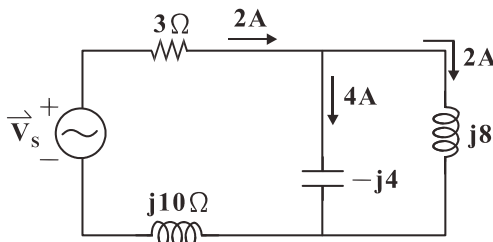


$$\vec{S} = I^2 \vec{Z} = 2^2(3 + j2) = 12 + j8 = 14.42 \angle 56.31^\circ$$

$$P.F. = \frac{12}{14.42} = 0.83 \text{ (落後) L 性}$$

$$19. \quad R = 250 \times 10^\circ \Omega \pm 1\% = 250 \Omega \pm 2.5 \Omega$$

$$P = \frac{5^2}{250} = 0.1W$$

20.

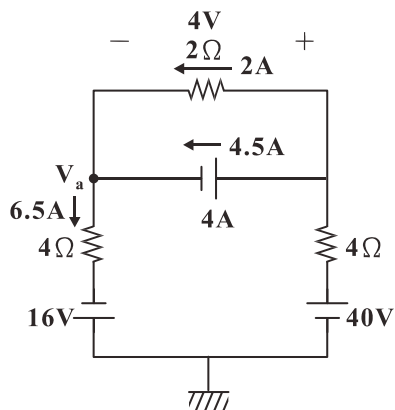

$$V_a = (2 + 4.5) \times 4 - 16 = 10V$$

21. $V_{PP} = 2V_m = 2 \times 6 = 12V$


$$\frac{12}{6} = 2V/DIV$$

$$f = \frac{157}{2\pi} = 25Hz$$

$$T = \frac{1}{f} = \frac{1}{25} \text{ 秒} = 40 \text{ 毫秒}$$


$$\frac{40ms}{8} = 5ms/DIV$$

22.

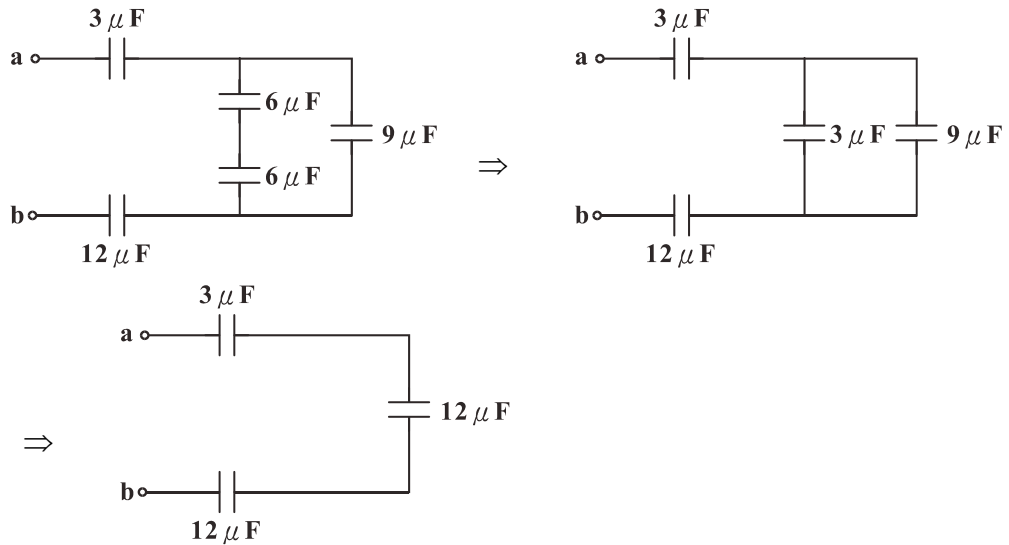

$$\frac{1}{C_{ab}} = \frac{1}{3} + \frac{1}{12} + \frac{1}{12} = \frac{1}{2}, \quad C_{ab} = 2 \mu F$$

23.

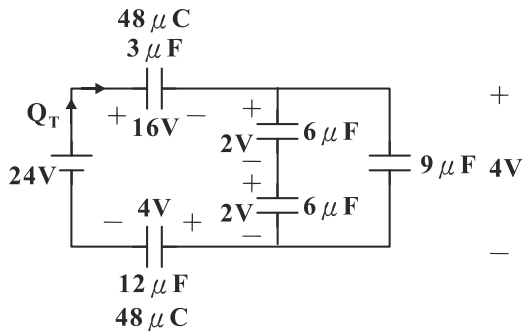

$$Q_T = 24 \times 2 = 48 \mu C$$

24. RL 並 $\Rightarrow$ L 性

$i_s(t)$ 落後 $v_s(t)$ θ 角

$i_R(t)$ 與 $v_s(t)$ 同相

$i_L(t)$ 落後 $v_s(t)$ 90°


25. 指示燈接線脫落，指示燈與電熱線並聯。

$$26. \quad V_{o(av)} = 110 \times \frac{12}{110} \times \sqrt{2} \times \frac{2}{\pi} = \frac{24\sqrt{2}}{\pi} \text{ V}$$

$$PIV = 1V_{2m} = 110 \times \frac{12}{110} \times \sqrt{2} = 12\sqrt{2} \text{ V}$$

27. 主動區 — $\begin{cases} \text{E-B : 順向} \\ \text{C-B : 逆向} \end{cases}$

$$\therefore V_E > V_B > V_C$$

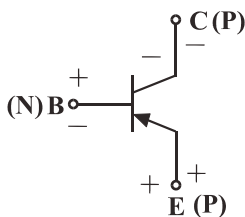

$$28. \quad \therefore \beta I_B = 150 \times 1\text{mA} = 150\text{mA}$$

$\therefore \beta I_B > I_C$ ，可知 BJT 飽和

$$29. \quad V_{BB} = 12 \times \frac{50\text{k}}{450\text{k} + 50\text{k}} + (-12) \times \frac{450\text{k}}{50\text{k} + 450\text{k}} = -9.6\text{V}$$

$$R_B = 450\text{k} // 50\text{k} = 45\text{k}\Omega$$

$$I_B = \frac{V_{BB} - V_{BE} - V_{EE}}{R_B + (1 + \beta)R_E} = \frac{-9.6 - 0.7 - (-12)}{45\text{k} + (1 + 54) \times 1\text{k}} = 0.017\text{mA}$$

$$I_C = \beta I_B = 54 \times 0.017\text{mA} = 0.918\text{mA}$$

$$V_C = V_{CC} - I_C R_C = 12 - 0.918\text{mA} \times 5\text{k} = 7.41\text{V}$$

$$30. \quad A_V = \frac{V_o}{V_i} = -\beta \times \frac{R_C // R_{F2}}{r_\pi} = -100 \times \frac{3\text{k} // 68\text{k}}{1\text{k}} \doteq -287$$

31. dB 值為負值，表示 $|A_V| < 1$ $\therefore |V_o| < |V_i|$

32. P 通道 MOSFET — $\begin{cases} \text{基底為 N 型} \\ \text{S 極與 D 極為 P 型} \end{cases}$

$$33. \quad A_V = \frac{V_o}{V_i}$$


$$= g_m(R_D // R_L)$$

$$= 4\text{m} \times (2\text{k} // 10\text{k})$$

$$= 6.66$$

$$A_i = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_i}{R_S // \frac{1}{g_m}}} = A_V \times \frac{R_S // \frac{1}{g_m}}{R_L}$$
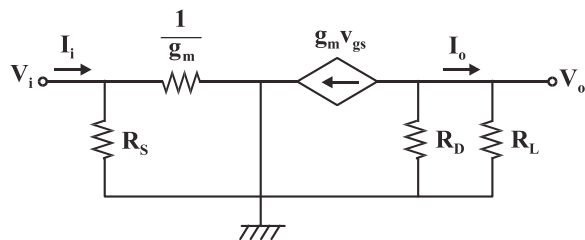
$$= 6.66 \times \frac{1\text{k} // \frac{1}{4\text{m}}}{10\text{k}} = 0.1332$$



$$34. V_{GS1} = V_{GG} = 5V$$

$$I_{D2} = I_{D1} = K_1(V_{GS1} - V_{t1})^2 = 4m \times (5 - 3)^2 = 16mA$$

$$g_{m1} = 2\sqrt{K_1 I_{D1}} = 2\sqrt{4m \times 16m} = 16mA/V$$

$$g_{m2} = 2\sqrt{K_2 I_{D2}} = 2\sqrt{1m \times 16m} = 8mA/V$$

$$A_V = \frac{V_o}{V_i} = -g_{m1} \times \left(\frac{1}{g_{m2}} // R_L \right) = -16m \times \left(\frac{1}{8m} // 10k \right) \div -1.98$$

$$35. I_D = \frac{V_{DD} - V_{DS}}{R_D + R_S} = \frac{15 - 7.5}{2k + 1k} = 2.5mA$$

$$V_{GS} = V_P \times \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -3 \times \left(1 - \sqrt{\frac{2.5m}{10m}} \right) = -1.5V$$

$$V_G = V_S + V_{GS} = I_D \times R_S + V_{GS} = 2.5m \times 1k - 1.5 = 1V$$

$$\frac{V_G}{V_{DD}} = \frac{R_G}{210k + R_G}, \text{ 即 } \frac{1}{15} = \frac{R_G}{210k + R_G}$$

$$\therefore R_G = 15k\Omega$$


$$36. g_m = \frac{2I_{DSS}}{|V_P|} \times \left(1 - \frac{V_{GS}}{V_P} \right) = \frac{2 \times 10m}{3} \times \left(1 - \frac{-1.5}{-3} \right) = 3.3mA/V$$

$$A_V = \frac{-g_m(R_D // R_L)}{1 + g_m R_S} = \frac{-3.3m \times (2k // 10k)}{1 + 3.3m \times 1k} = -1.28$$

$$37. Y = \overline{[(A \cdot B) + (C \cdot D)] \cdot E} = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) + \bar{E}$$

$$38. \text{ 令 } R = 1\Omega, \text{ 且 } V_i = 1V$$
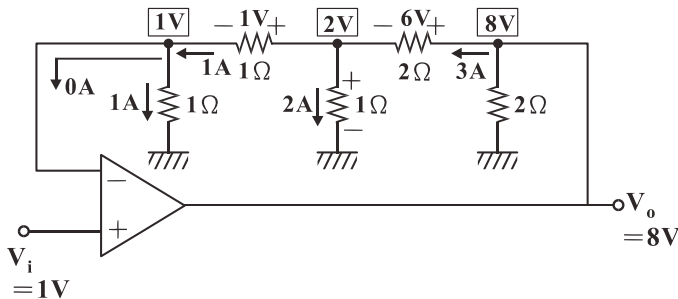
$$A_V = \frac{V_o}{V_i} = \frac{8V}{1V} = 8$$



$$39. V_o = -\left[\frac{60k}{30k} \times (-3) + \frac{60k}{20k} \times (-2) + \frac{60k}{10k} \times 2 \right] + \left[\left(\frac{2}{20k} + \frac{1}{10k} \right) \times (20k // 10k // 20k) \right] \times \left(1 + \frac{60k}{30k // 20k // 10k} \right)$$

$$= 0 + 12 = 12V$$

$$40. V_U = 15 \times \frac{2k}{18k + 2k} + 1 \times \frac{18k}{2k + 18k} = 2.4V$$

$$V_L = -15 \times \frac{2k}{18k + 2k} + 1 \times \frac{18k}{2k + 18k} = -0.6V$$

41. $V_R=0V$ 時：

$$V_U = \frac{2k}{18k+2k} \times 15 = 1.5V$$

$$V_L = \frac{2k}{18k+2k} \times (-15) = -1.5V$$

$$\therefore V_i(t) = 3\sin(100t)V \begin{cases} +V_{ip} = 3V > 1.5V \\ -V_{ip} = -3V < -1.5V \end{cases}$$

$\therefore V_o$ 為方波

43. $\therefore V_{r(P-P)} = \frac{V_P}{2f_s R_L C}$ $\therefore C$ 值愈大，輸出漣波電壓 $V_{r(P-P)}$ 值愈小。

44. $I_{Z(max)} = \frac{P_{Z(max)}}{V_Z} = \frac{150mW}{10V} = 15mA$

$$I_L = \frac{V_Z}{R_L} = \frac{10}{1k} = 10mA$$

$$\begin{cases} I_{R(min)} = I_{Z(min)} + I_L = 2m + 10m = 12mA \\ I_{R(max)} = I_{Z(max)} + I_L = 15m + 10m = 25mA \end{cases}$$

$$\begin{cases} R_{(max)} = \frac{V_S - V_Z}{I_{R(min)}} = \frac{16-10}{12m} = 500\Omega \\ R_{(min)} = \frac{V_S - V_Z}{I_{R(max)}} = \frac{16-10}{25m} = 240\Omega \end{cases}$$

45. (1) $V_{EE} = V_{BE} + I_E R_E = 0.7 + 1.3m \times 8k = 11.1V$

(2) $\alpha = \frac{\beta}{1+\beta} = \frac{199}{1+199} = 0.995$

$$r_e = \frac{V_T}{I_E} = \frac{26mV}{1.3mA} = 20\Omega$$

$$A_v = \frac{V_o}{V_i} = \alpha \times \frac{R_C // R_L}{r_e} = 0.995 \times \frac{6k // 6k}{20} = 149.25$$

46. ENMOS 飽和區 $\begin{cases} V_{GS} > V_t \\ V_{GD} < V_t \\ V_{DS} \geq V_{GS} - V_t \end{cases}$

選項(C)： $V_{GS}=3V$ ， $V_{DS}=1.5V$ ，而 $V_t=2.5V$

$$\therefore V_{GD} = V_{GS} - V_{DS} = 3 - 1.5 = 1.5V，而 V_{GS} - V_t = 3 - 2.5 = 0.5V$$

$$\therefore \begin{cases} V_{GS} > V_t (3V > 2.5V) \\ V_{GD} < V_t (1.5V < 2.5V) \\ V_{DS} > V_{GS} - V_t (1.5V > 0.5V) \end{cases}$$

$$47. \quad I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 - 6}{1.2k} = 5mA$$

$$K = \frac{I_D}{(V_{GS} - V_t)^2} = \frac{5m}{(2.5 - 2)^2} = 20mA/V^2$$

$$48. \quad f_H = \frac{1}{2\pi R_A C_A} = \frac{0.1592}{0.5k \times 0.01\mu} = 31.84kHz$$

$$f_L = \frac{1}{2\pi R_B C_B} = \frac{0.1592}{1k \times 0.05\mu} = 3.184kHz$$

$$BW = f_H - f_L = 31.84k - 3.184k \doteq 28.66kHz$$

$$49. \quad f_o = \frac{1}{2RCI_n(1 + \frac{2R_2}{R_1})} = \frac{1}{2 \times 50k \times 0.2\mu \times I_n(1 + \frac{2 \times 8.5k}{10k})} = 50Hz$$

$$50. \quad f_o = \frac{1}{2\pi\sqrt{6}RC} = \frac{0.065}{10k \times 0.01\mu} = 650Hz$$

$$R_2 = 29 \times R_1 = 29 \times 20k = 580k\Omega$$